



Verilog SystemVerilog training

RTL approach

A g e n d a

Verilog Systemverilog training course for RTL

Students are expected to have basic knowledge on Boolean algebra, some logic gates and K-map.

Step 1

Basic

RTL designer
introduction.
Basic logic component
Basic syntaxes

Step 2

Advance

More languages'
syntaxes.
Design training and
coached small project.

P r o s & C o n s o f

Digital system

“Systems which process discrete values are called digital systems. In digital representation the quantities are represented not by proportional quantities but by symbols called digits.”


--- Deepak Kumar Tala, asic-world

- Easy to design
- Digital system only cares about value (HIGH or LOW), not the exact voltage.
- Easy to store information.
- Programmable.
- Less affected by noise. Size is smaller (more logic can be fabricated in to 1 IC

- Most signals in real world are analog. Thus, there is a need to convert the signals to digital.

Simple flow

Digital design

 

1. Front End (FE)

Requirements from user and designer are written in documents.

The design is implemented (e.g., RTL design)

The functionality of the designed is verified (Design Verification)

2. Middle End (ME)

Convert (Synthesize) the design to logic gate cells (netlist).

The speed (performance) of the netlist is verified (STA)


3. Back End (BE)

Place and Route (PnR) the logic gate cells.

The netlist is put in physical world (layout) with real cells and metal connection for manufacturing.


Flow of

Digital design

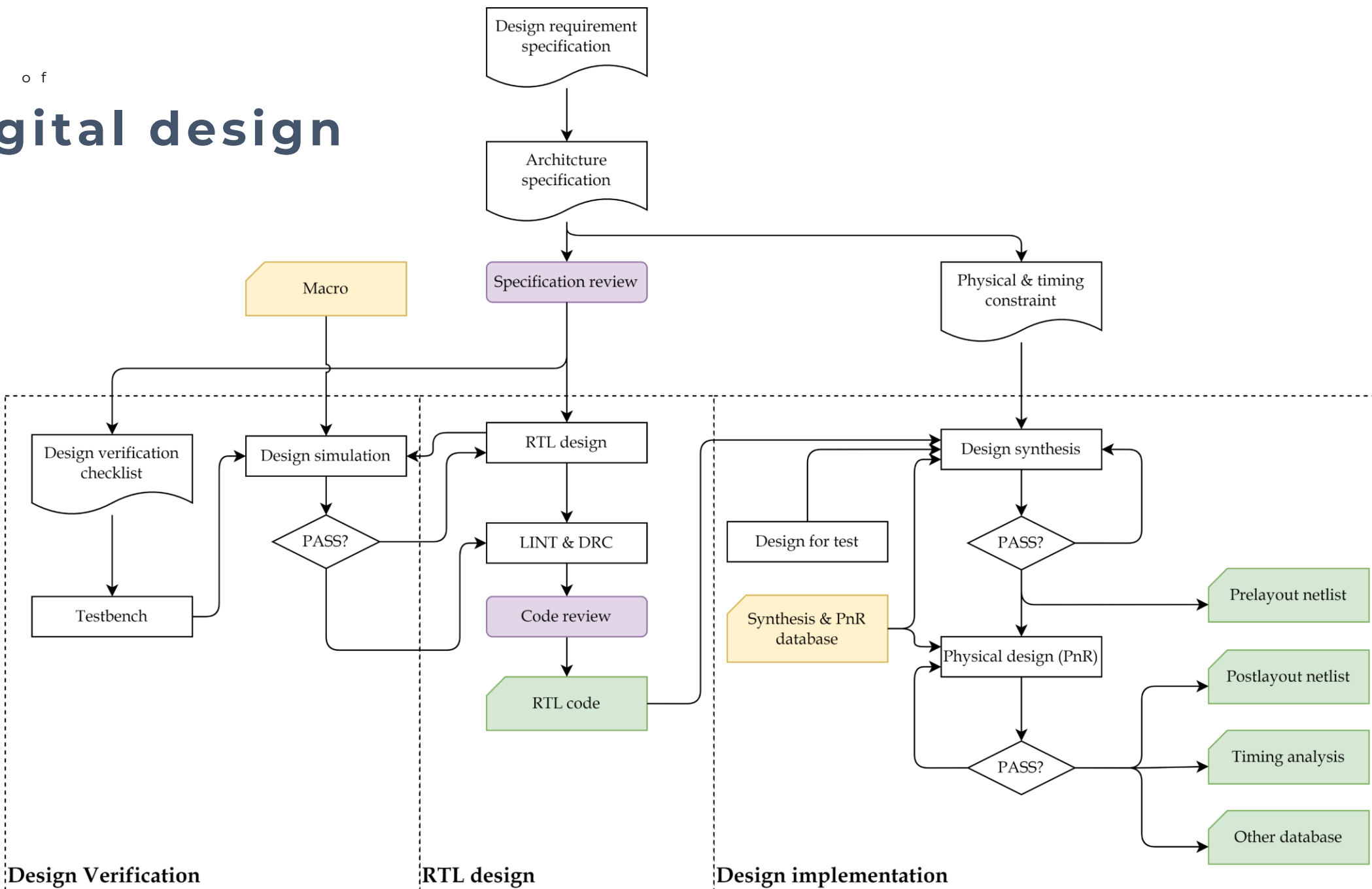


Training scope

Phase 1

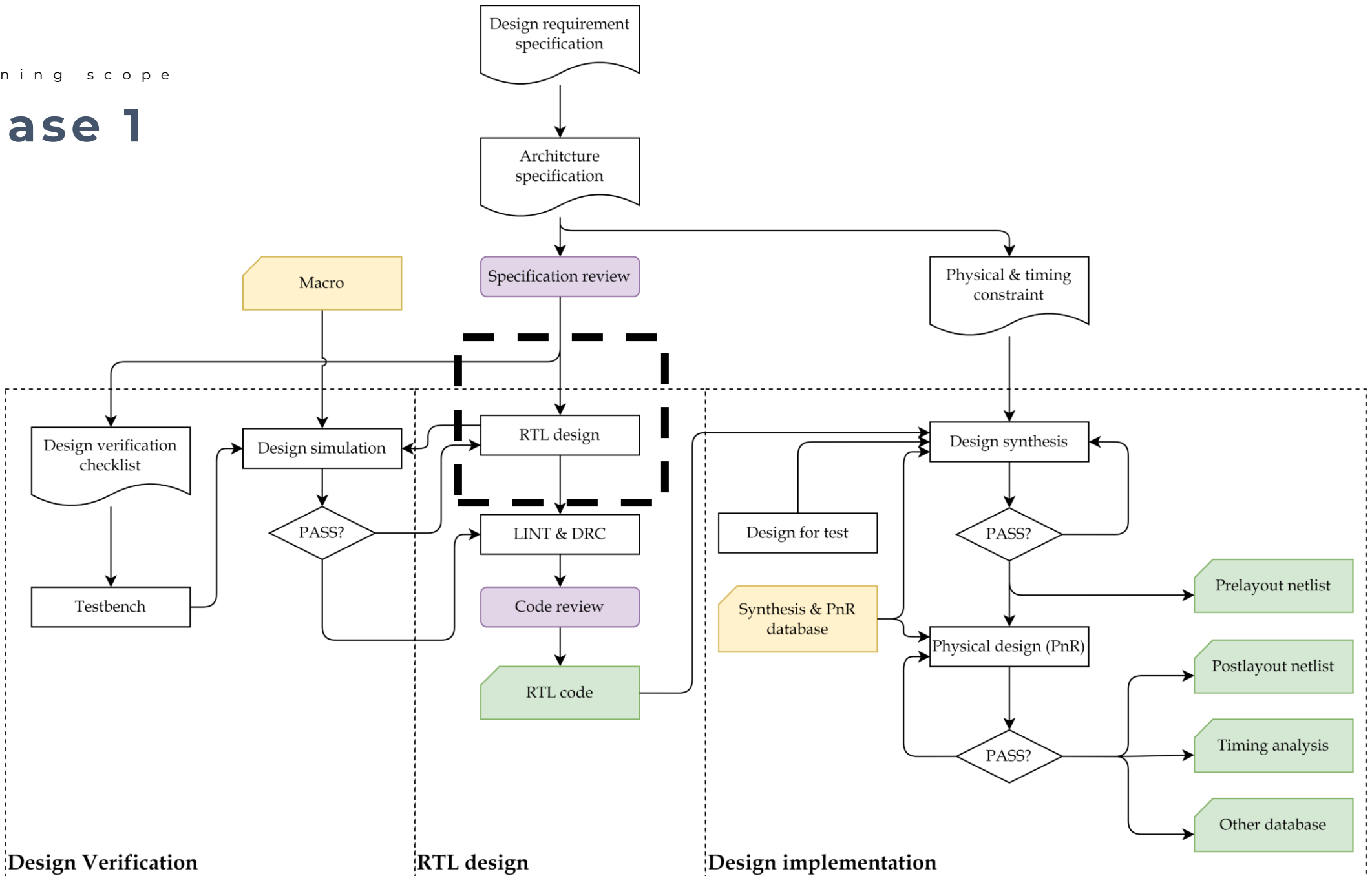

Training scope

Phase 2

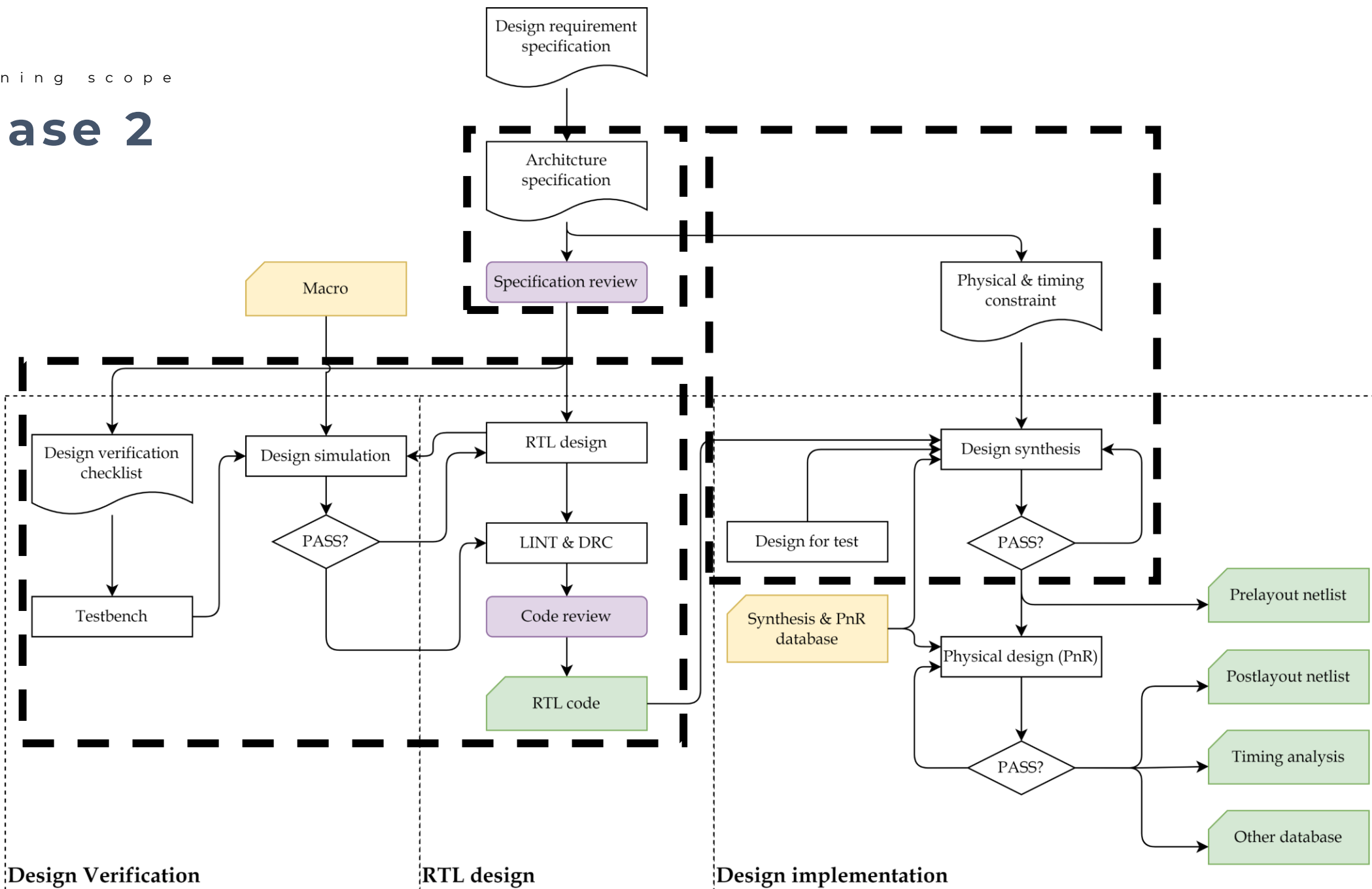

Expected

Training outcome

As Verilog language was first created to describe hardware (HDL), thus this program focuses more on RTL part.

What it provides:

- Understand RTL design concept: From specification, to design and writing code.
- Basic syntaxes of Verilog/SystemVerilog to work in daily life tasks.

Expected outcome:

- Understand simple snippets of RTL code. Has ability to write RTL for simple blocks.
- Has ability to debug syntax problems of RTL codes.
- Has ability to create simple test bench & run text-based simulation.



IMPORTANT

MYTH BUSTER

**RTL engineer is not Software engineer.
Writing Verilog is not programming.**




COMMON LOGIC CELLS

Please review functionality of combinational cells:
INV, AND, OR, XOR, MUX.
Following slides are about sequential logic cells.

D i g i t a l s y s t e m

Sequential circuit

 Most systems in practice include memory elements, which is one of sequential logic type.



There are 2 types of sequential logic cells:

- Latch: The output senses the level of the inputs to capture data.
- Flipflop: The output sense the edge of the inputs to capture data.

Commonly use are D-latch and D-flipflop



Data is captured by input's level

Pin E enables data to go through the latch.

E	D	Q
0	*	Q
1	0	0
1	1	1

Sequential logic cell

D-latch


 
 


Data is captured by input's edge
Rising edge of the clock captures input data.

CLK	D	RN	Q
*	*	0	0
0	*	1	Q
1	*	1	Q
R	0	1	0
R	1	1	1
F	*	1	Q

Sequential logic cell

D-flipflop

   

ACTIVITY


Check 3.1, 3.2

VERILOG, SYSTEMVERILOG SYNTAX

Basic syntax of the language.

S y n t a x

Module and Instance

 

Module: `dec`, `dec_tb`
Instance: `dut_ld`, `dut_fl`

```
// file: dec.v
module dec (
    // Ports of the DUT
    input wire rst_n
    , input wire [3:0] code_in
    , output wire [3:0] code_out
    , input wire [1:0] dec_in
    , output wire [1:0] dec_out
);

endmodule // dec
```

```
// file: dec_tb.v
module dec_tb;

    // Signals of the testbench
    wire [1:0] dec_ltf;
    wire [1:0] dec_ftl;
    reg [3:0] ld_code_in;
    wire [3:0] ld_code_out;
    reg [3:0] fl_code_in;
    wire [3:0] fl_code_out;
    reg rst_n;

    // Instances of the DUT
    dec dut_ld (
        .rst_n ( rst_n )
        , .code_in ( ld_code_in )
        , .code_out( ld_code_out )
        , .dec_in ( dec_ftl )
        , .dec_out ( dec_ltf )
    )
    dec dut_fl (
        .rst_n ( rst_n )
        , .code_in ( fl_code_in )
        , .code_out( fl_code_out )
        , .dec_in ( dec_ltf )
        , .dec_out ( dec_ftl )
    )
endmodule // dec_tb
```


A module is a block of Verilog code that implements a certain functionality.

An instance is an object of the module. Each instance is a complete, independent, and concurrently active copy of a module.

S y n t a x


Port declaration

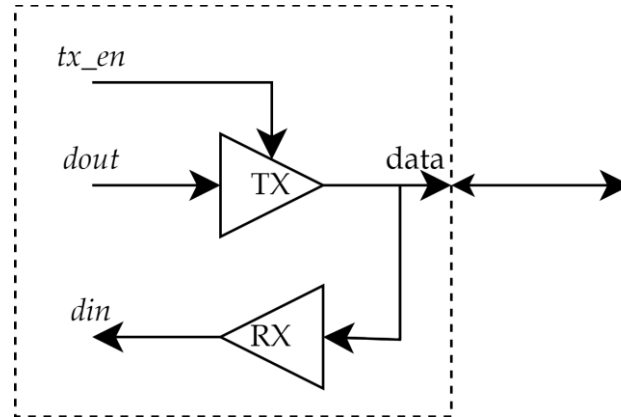input: tx_en, dout
output: din
inout: data



```
// file: dec.v
module dec (
    // Ports of the DUT
    input wire    rst_n
    , input wire [3:0] code_in
    , output wire [3:0] code_out
    , input wire [1:0] dec_in
    , output wire [1:0] dec_out
);

endmodule // dec
```

 

Inout ports are ports that can be either input or output depend on the configuration.
In Verilog, there are rules to define data type & connect data types to the ports. The data types are explained later.

Data type

Type	Commonly use	Description
Net	wire	Structural connection between components. It does not hold value.
Register	reg	Represent variables that are used to store data.

A wire get its' value through assign

A reg get its' value in a procedural block such as always

```
module and4 (  
    input wire [3:0] din  
    , output wire      dout  
);  
  
assign dout = din[0]&din[1]&din[2]&din[3];  
  
endmodule //and4
```

```
module dff (  
    input wire rst_n  
    , input wire clk  
    , input wire din  
    , output reg dout  
)  
  
always @(posedge clk or negedge rst_n) begin  
    if (!rst_n) dout <= 1'b0;  
    else dout <= din;  
end  
  
endmodule //dff
```

When converting between code and schematic, a wire can be understood as real connection between components, it is a true wire to connect ports.

However, reg does not always represent sequential components as shown in DFF example.

C o m m o n m i s t a k e

wire and reg

MUX cell

dout is reg type, the variable stores data but the functionality is not. There is no case that dout can keep its' data.

```
module mux2(  
    input wire sel  
    , input wire din_0  
    , input wire din_1  
    , output reg dout  
);  
  
always @(sel or din_0 or din_1) begin  
    if (sel==1'b0) dout = din_0;  
    else dout = din_1;  
end  
  
endmodule //mux2
```

Latch cell

dout is reg type, the variable stores data and the function does to. It stores data when en is 0.

```
module latch(  
    input wire en  
    , input wire din  
    , output reg dout  
);  
  
always (en or din) begin  
    if (en) dout = din;  
end  
  
endmodule //latch
```

ACTIVITY

Check 4.1, 4.2

FLEXIBLE DATA SIZE

When designing hardware, we can declare variables with a range (normally we call them bus). The language does support fixed size data type such as integer.

Unlike most programming languages, Verilog allows us to interact with each bit.

IMPORTANT NOTE


Data size

```
wire [1:0] a;  
wire [3:0] b;  
assign a[1] = 1'b1; // Assign different value for a[0] and a[1]  
assign a[0] = 1'b0;  
assign b[3:2] = a; // Assign value of 'a' to a range of bus b  
assign b[1] = a[0]; // Assign bit by bit for bus b  
assign b[0] = a[1];
```

Data value

Value	Description
0	Logic zero or false
1	Logic one or true
X	Unknown logical value
Z	The high impedance of the tri-state gate

 inout port is HiZ if the driver is disabled.



```
assign data = dout1;
assign data = dout2;
```

dout1	dout2	data
1	1	1
0	0	0
Z	*	dout2
*	Z	dout1
1	0	X
0	1	X

Unknown value is where the value can't be identified as the other 3 values.

S y n t a x

Arithmetic Operator

Operator Type	Operator Symbol	Operation Performed
Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
	+	Unary plus
	-	Unary minus

**Same as C programming
language.**

S y n t a x

Logical Operator

Operator Type	Operator Symbol	Operation Performed
Logical	!	Logical negation
	&&	Logical and
		Logical or

The result is true or false as in most programming language

```
if (a) // True if a is not 0
if (!a) // True if a is 0
if (a&&b) // True if both a and b are not 0
if (a||b) // True if a or b is 0
```


S y n t a x

Relational Operator

Operator Type	Operator Symbol	Operation Performed
Relational	>	Greater than
	<	Less than
	>=	Greater than or equal
	<=	Less than or equal

Same as other
programming language

S y n t a x

Equality Operator

Operator Type	Operator Symbol	Operation Performed
Equality	==	Equality
	!=	Inequality
	===	Equality, compare X and Z
	!==	Inequality, compare X and Z

**Same as other
programming language**

Unlike programming language, Verilog has value X and Z, thus it need “===” and “!==” to compare those value. Otherwise, it ignores the value.

S y n t a x

Reduction & bitwise Operator

Operator Type	Operator Symbol	Operation Performed
Reduction & bitwise	~	Bitwise negation
	&	and
	~&	nand
		or
	~	nor
	^	xor
	^~	xnor
	~^	xnor

Operators work on bit scale instead of the whole signal.

The operators & and | are different with the logical operator && and ||.

```
logic [2:0] a, b, c;
logic e;

initial begin
    a = 3'b101;
    b = 3'b011;
    c = ~a; // c = 3'b010
    e = |a; // e = 1'b1, reduction operation always result 1 bit
    c = a&b; // c = 3'b001;
    c = a|b; // c = 3'b111;
end
```

S y n t a x

Shift Operator

Operator Type	Operator Symbol	Operation Performed
Shift	>>	Right shift
	<<	Left shift

MSB in Right shift and
LSB in Left shift are
filled with 0.

Similar to C programming language.

```
logic [3:0] a;  
  
initial begin  
    a = 4'b0111;  
    a = (a<<2); // a = 4'b1100;  
    a = (a>>2); // a = 4'b0011;  
end
```

S y n t a x

Concatenation Operator

Operator Type	Operator Symbol	Operation Performed
Concatenation	{ }	Concatenation

Assign portion values of 1 bus.

In above example, {2{c}} mean signal c is duplicated 2 times.

```
logic [3:0] a, b;  
logic [1:0] c;  
logic [15:0] d;  
  
assign d = {a, c, b, {2{c}}, 2'b10};
```

S y n t a x

Conditional Operator

Operator Type	Operator Symbol	Operation Performed
Conditional	?	Conditional

Similar to if...else...
clause.

Mainly used for wire data type, where if...else clause is not permitted.

```
wire s0, s1;
wire i0, i1, i2, i3;
wire o;

// Select i* depends on s*
// - {s1, s0} = 2'b11, o = i3
// - {s1, s0} = 2'b10, o = i2
// - {s1, s0} = 2'b01, o = i1
// - {s1, s0} = 2'b00, o = i0
assign o = s1 ? (s0 ? i3 : i2) : (s0 ? i1 : i0);
```

S y n t a x

Procedural block

Procedural blocks are used to define behavior of a module. Register data types can get value from these blocks.

There are 2 types of procedural blocks:

- initial: Run once at the beginning of the simulation process. Don't use in RTL code because this does not reflect any hardware.
- always: Always runs since the simulation starts.

```
// begin...end is required if 1 block has more than 1 assignment  
initial begin  
    rst_n = 1'b0;  
    ld_code_in = 4'b0000;  
    fl_code_in = 4'b0000;  
end
```

```
reg clk;  
  
// This block does not use begin...end because it only has 1 assignment  
initial clk = 0;  
always #50ns clk = ~clk;
```




EXAMPLE: COUNTER

This example shows how to develop
testbench and simulation result.

E x a m p l e

Counter


Port name	Size	Description
clk	1	Clock, active at risign edge
rst_n	1	Asynchronous reset, counter is reset to 0 whenever this signal is 0
en	1	Synchronous enable, counter can only count up when this signal is 1
cnt_out	4	Counter output

 

- At T0, cnt_out is undefined since it is starting point of simulation.
- T2: cnt_out is reset to 0 when rst_n = 0
- T4: en = 1 when rst_n = 0 so there is no change on cnt_out
- T6: en = 1 when rst_n = 1 so cnt_out starts counting up.
- T11: en = 0 so cnt_out is unchanged


S y n t a x

Blocking assignment

 

```
always @(a) begin
    b = a;
    c = b;
end
```

Blocking assignment waveform

 


Use to represent
combinational logic &
latch

Blocking assignments are executed in order as they are coded. Each assignment blocks the next one until it is executed, thus the assignment is called *blocking*. They are made with "=", e.g. a=b


S y n t a x

Nonblocking assignment

 

```
always @(posedge clk) begin
    b <= a;
    c <= b;
end
```

Use to represent flip flop

 

Nonblocking assignments are executed in parallel. They do not block each other thus they are called *nonblocking*. They are made with "<=", e.g., a<=b



IMPORTANT

COMMON MISTAKE

RACING CONDITION

C o m m o n m i s t a k e

Racing condition

Mostly happens with
non blocking
assignment

```
always @(a) b = a;  
always @(a) c = b;
```

Racing, c is
unpredictable when a
changes value

```
initial b = 0;  
initial b = 1;
```

Racing, b is
unpredictable at the
beginning of simulation

```
always @(posedge clk) b <= a;  
always @(posedge clk) c <= b;
```

Not racing, this follows
RTL coding rules and
represents 2 serial
flipflop

When there are 2 or more assignments happen at the same time, simulation tools can't define which assignment happens first and racing happens. It depends on tools' algorithm and the code to make order and it is unpredictable.

ACTIVITY

Check 4.3

S y n t a x

if...else statement

Why do we need first
assignment for out &
hit?

The syntax is not different with programming languages.

```
module encoder (  
    input wire [3:0] in  
    , output reg [1:0] out  
    , output reg hit  
);  
  
always @(in) begin  
    out = 2'd0;  
    hit = 1'b0;  
    if (in==4'b0001) begin  
        out = 2'd0;  
        hit = 1'b1;  
    end else if (in==4'b0010) begin  
        out = 2'd1;  
        hit = 1'b1;  
    end else if (in==4'b0100) begin  
        out = 2'd2;  
        hit = 1'b1;  
    end else if (in==4'b1000) begin  
        out = 2'd3;  
        hit = 1'b1;  
    end  
end  
endmodule
```

S y n t a x

case statement

case statement is used when there are too many branches.

If we don't care about other bits, case can be written as:

casez (a)

2'b?1: // True if bit [0] is 1, regardless value of bit[1]

2'b10: // True if bit [0] is 0 and bit [1] is 1

default: // Remaining cases

endcase

However, casez and casex are not recommended in RTL code because they allow Z and X values.

```
module decoder (  
    input wire [1:0] in  
    , output reg [3:0] out  
);  
  
always @(in) begin  
    case (in)  
        2'b00 : out = 4'b0001;  
        2'b01 : out = 4'b0010;  
        2'b10 : out = 4'b0100;  
        2'b11 : out = 4'b1000;  
    endcase  
end  
  
endmodule
```


S y n t a x

for loop statement

for loop is the same as
other languages.

The example is used in test bench

```
module decoder_tb;
  reg [1:0] in;
  wire [3:0] out;

  int idx;

  initial begin
    $display("Initial the design");
    $monitor("Monitor: %t in: %d, out: %b", $realtime, in, out);
    #5ns in = 2'd0;
    for (idx=0; idx<4; idx=idx+1) begin
      #5ns in = idx;
    end
    $display("Reach final value");
  end

endmodule
```

ACTIVITY

Check 4.4

repeat & wait statements

repeat runs a statement in a defined number of times.

wait is a level condition that hold execution until it is true.

The example is used in test bench

```
initial begin
    idx = 0;
    repeat (4) begin
        #5ns in = idx;
        idx = idx+1;
    end
end

initial begin
    $display("Initial the design");
    $monitor("Monitor: %t in: %d, out: %b", $realtime, in, out);
    wait (idx==4) $display("Reach final value");
end
```

System tasks & function

They are predefined by the language. Some of them can be also use for RTL code.

- `$display` and `$strobe` display once every time they are executed.
- `$monitor` displays every time one of its parameter changes.
- `$finish` exits the simulator back to the operating system.
- `$random` generates a random integer every time it is called.
- `$realtime` returns the current simulation time as a real number

begin...end: Sequential block
fork...join: Parallel block

```
// file: sequential_tb
module sequential_tb;
    reg [1:0] idx;

    initial begin
        $monitor("Monitor: %t idx: %d", $realtime, idx);
        // Each assignment blocks the latter ones
        #5ns idx = 0;
        #10ns idx = 1;
        #15ns idx = 2;
    end

endmodule
```

```
Monitor:           0 idx: x
Monitor:          5000 idx: 0
Monitor:         15000 idx: 1
Monitor:         30000 idx: 2
```

```
// file: parallel_tb
module parallel_tb;
    reg [1:0] idx;

    initial begin
        $monitor("Monitor: %t idx: %d", $realtime, idx);
        // All assignments run at once
        fork
            #5ns idx = 0;
            #10ns idx = 1;
            #15ns idx = 2;
        join
    end

endmodule
```

```
Monitor:           0 idx: x
Monitor:          5000 idx: 0
Monitor:         10000 idx: 1
Monitor:         15000 idx: 2
```

V e r i f i c a t i o n S y n t a x

Procedural assignment group

S y n t a x

Procedural timing control

```
#<time> statement;
```

```
<signal 1> = #<time> <signal 2>;
```

```
#5ps a = 1; // a = 1 at 5ps  
b = 0;      // b = 0 at 5ps  
#10ps;  
a = #5ps 0; // a = 0 at 20ps.  
b = 1;      // b = 1 at 15ps
```

```
@([<posedge>|<negedge>] <signal>) <statement>;
```

```
wait (<expression>) <statement>;
```

Timing for procedural
blocks is introduced
across the document.

- Delay controls.
- Edge-Sensitive Event controls.
- Level-Sensitive Event controls-Wait statements.

S y n t a x

Directive

```
`define <MACRO>
```

```
`define display_info(message) $display("%m [INFO]    %t %s %d: %s", $realtime, `__FILE__, `__LINE__, message)  
...  
initial #1200 `display_info("Test message");
```

**Directives are guidance
for tool to compile the
source code.**

Simulation tools do at least 2 steps:

- Compile code into a database
- Simulate the code

```
`ifdef <NAME>  
`else  
`endif
```

```
initial begin  
`ifdef FIRST  
    $display("FIRST");  
`else  
`ifdef SECOND  
    $display("SECOND");  
`else  
    $display("NONE");  
`endif  
`endif  
end
```

S y n t a x

Parameter

```
module counter_param #(
    pCOUNTER_WIDTH = 4; // Default value of the counter
) (
    input wire          clk
    , input wire        rst_n
    , input wire        cnt_en
    , output reg [pCOUNTER_WIDTH-1:0] cnt_out
);
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) cnt_out <= 0;
        else if (cnt_en) cnt_out <= cnt_out + 1'b1;
    end
endmodule
```

```
counter_param #(
    .pCOUNTER_WIDTH(8)
) u_dut (
    clk      ( clk      )
    , rst_n  ( rst_n    )
    , cnt_en ( cnt_en    )
    , cnt_out(cnt_out   )
);
```

A module with parameters allow the instances to be different.

The simplest example for parameter is capacitors have the same function, but they have different capacitance values.

S y n t a x

Task

A task does a common set of steps that other parts of the code can call it

Task is only used in testbench

```
task compare;
input  [1:0] drv_in;
input  [3:0] exp_out;
output          error;
begin
    error = 1'b0;
    #5ns in = drv_in; // Task can drives the global variable
    #5ns if (out!=exp_out) begin
        $display("Data is unexpected out:%b exp:%b", out, exp_out);
        error = 1'b1;
    end
end
endtask
```

Function

```
assign a[0] = c[0] ? b[0] : b[1];  
assign a[1] = c[1] ? b[1] : b[2];  
assign a[2] = c[2] ? b[2] : b[3];
```

```
function [2:0] muxing;  
  input [2:0] sel;  
  input [3:0] din;  
  integer idx;  
  begin  
    for (idx=0;idx<3;idx=idx+1)  
      muxing[idx] = sel[idx] ? din[idx] : din[idx+1];  
    end  
  endfunction
```

A function is a replacement for a combinational logic (can be used in RTL code), while task replaces for a routine (like in testbench).

- A function definition cannot contain any time-controlled statements—that is, any statements introduced with #, @, or wait.
- Functions cannot enable tasks.
- A function definition must contain at least one input argument.
- A function definition must include an assignment of the function result value to the internal variable that has the same name as the function.
- A function definition can not contain an inout declaration or an output declaration

FINITE STATE MACHINE (FSM)

Explanation & example

Definition

“FSM [...] is an abstract machine that can be in exactly one of a finite number of states at any given time. The FSM can change from one state to another in response to some inputs; the change from one state to another is called a transition.”

--- Wikipedia

FSM is not syntax; it is a digital design.



Safe

State: Locked, Unlocked

Transition:

- Correct combinations, state transfer to Unlocked
- Wrong: Reset to initial Locked



Traffic light


State: Green, Yellow, Red

Transition: State changes after a given time.

F S M t y p e s

Mealy & Moore

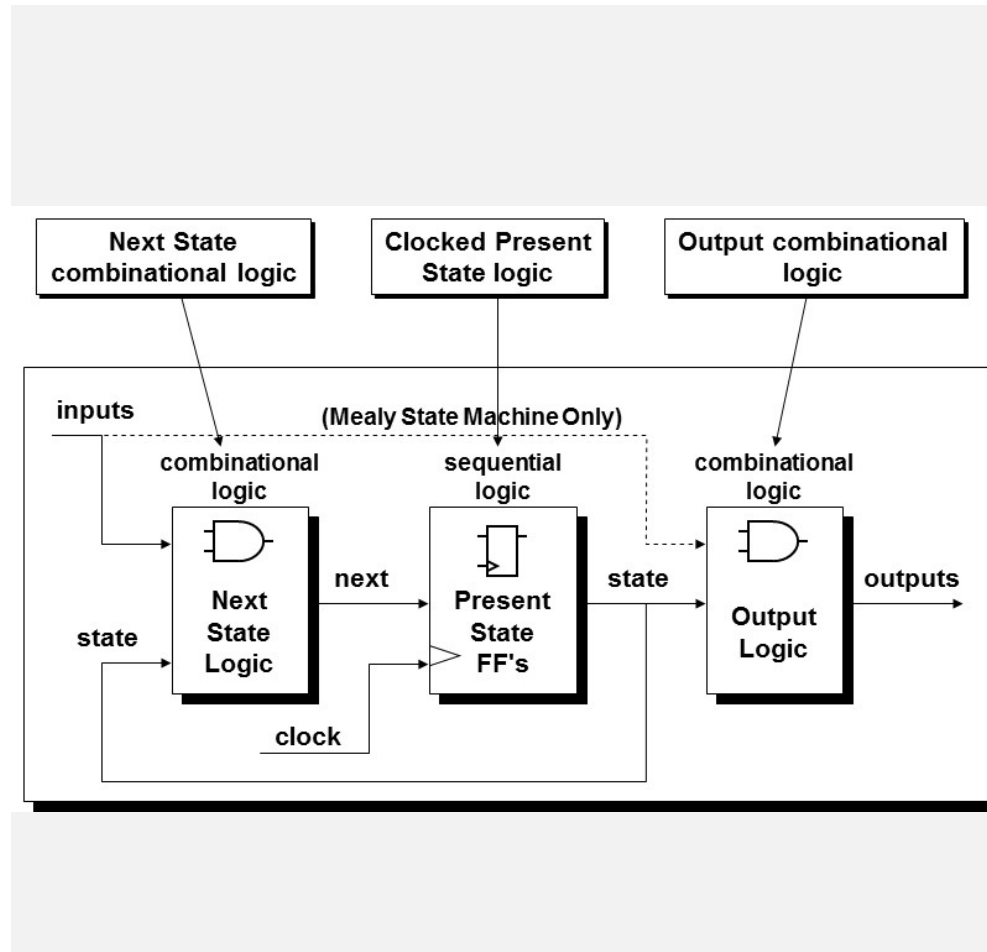Only use Moore version
unless it is undoable.



Moore state machine:
outputs are only a function
of the present state.
Mealy state machine: have
one or more outputs that
are a function of the
present state and one or
more inputs.

Figure credit: Clifford E. Cummings, posted in SNUG

E x a m p l e

Binary bit stream

Port name	Size	Description
clk	1	Clock, active at risign edge
rst_n	1	Asynchronous reset, counter is reset to 0 whenever this signal is 0
din	1	input
lock	1	output

The output lock asserts when din data matches with the sequence 1001, it keeps at high if the data repeat the sequence, for example 1001100110.... It is low if din has unexpected value

SystemVerilog

SystemVerilog is an expansion of Verilog. It supports both RTL and Verification teams to solve a lot of problems when working with Verilog.

ACTIVITY

Check 4.6

S y n t a x

always blocks

```
always_ff @(posedge clk or negedge rst_n)
    <code to describe flipflop function>
```

```
always_latch
    <code to describe latch function>
```

```
always_comb
    <code to describe combinational logic function>
```

**3 types of always block for
3 different functions.**

- always_ff is used for flipflop.
- always_latch is used for latch.
- always_comb is used for combinational logic.

S y n t a x

Logic datatype

```
logic a;  
initial #5 a = 1;  
initial #5 a = 0;
```

**logic can replace reg and
most of wire cases.**

- A *logic* variable can't be driven by multiple sources at the same time. (Example assert an error message)
- *logic* data type can't be assign to "inout" port.

S y n t a x

Assigning all bits

```
logic [2:0] a;  
  
initial begin  
    a = '1; // a = 3'b111;  
    a = 'x; // a = 3'bxxx;  
end
```

There are many cases that engineer want to assign all bits to the same value.

- '0 : Set all bits to 0
- '1: Set all bits to 1
- 'X or 'x : Set all bits to x
- 'Z or 'z : Set all bits to z

S y n t a x

Packed array

```
wire a [2:0]; // 3 elements array, each has 1 bit  
wire [3:0] b [5:0]; // 6 elements array, each has 4 bits
```

```
logic [5:0][3:0] b;  
  
initial begin  
    b = 18'ha_b_c_d_e_f; //b[5]=4'ha, b[4]=4'hb, etc.  
    b[5] = 4'h0; // b = 18'h0_b_c_d_e_f  
    b = (b<<1); // b = 18'hb_c_d_e_f_0  
end
```

Verilog only has 1 type of array.
SystemVerilog has packed and unpacked array.


Packed array works the same as bus in Verilog with additional dimensions.

S y n t a x

Naming block

Block naming helps reading
& debugging the code
easier.
 
```
module mdl_name();  
...  
endmodule : mdl_name  
  
task tsk_name();  
...  
endtask : tsk_name  
  
initial begin : blk_name  
...  
end : blk_name
```



If ending name does not match beginning name, it is an error.

S y n t a x


Enumeration data type

```
enum integer {IDLE=0, GNT0=1, GNT1=2} state; // define base type as integer, and initialize each state's value
enum integer {RED, GREEN, ORANGE} color; // Automatically assign value. RED=0, GREEN=1, ORANGE=2
enum integer {BRONZE=4, SILVER, GOLD} medal; // The first value is 4, thus the next ones are 5 & 6
```

```
enum {BRONZE=4, SILVER, GOLD} medal;
enum {GOLDEN} medal_ex;

initial medal = GOLDEN; // This will result in an error
```

enum is useful in FSM

 

enum is better than parameter for FSM:

- We can't assign an enum to names that are not defined in the declaration.
- Tools display enum as name, not just value thus it is much easier to debug.
- enum in EDA tool is shown as name instead of value as default.

S y n t a x

Struct data type

struct is used to group signals that have related function.

It can be used for ports too.

```
struct packed {  
    logic a;  
    logic [1:0] b;  
    logic c;  
} struct_eg;  
  
initial begin  
    struct_eg = '{a:1'b1, default:0}; // all bits except a are 0  
    struct_eg.b = 2'b11; // assign b to 1  
    struct_eg[0] = 1'b1; // assign c to 1  
end
```

```
// To reuse a set of enum and struct, we have to define  
// them first using typedef  
typedef logic [1:0] enum {  
    GREEN  
    , YELLOW  
    , RED  
} state_t;  
typedef struct packed {  
    logic init;  
    logic [2:0] light;  
} signal_t;  
  
state_t current_state, next_state;  
signal_t current_sig, next_sig;
```

S y n t a x

Enhanced task and function

function now can have
struct data type.

```
typedef struct packed {  
    logic hit;  
    logic [1:0] code;  
} pe_t;  
  
function automatic pe_t pe (  
    input [4:0] in  
);  
    integer idx;  
  
    pe = '{default:0};  
    for (idx=0; idx<5; idx=idx+1) begin  
        if (in[idx]==1'b1) begin  
            pe.hit = 1'b1;  
            pe.code = idx;  
            return pe;  
        end  
    end  
  
    return pe  
endfunction : pe
```

Some enhancements:

- automatic is for dynamic memory. In Verilog, they use static memory and cause troubles when there are more than one code call them at one time.
- Remove begin...end
- struct can be used for function, so now function can return more than 1 output.
- function now has return keyword to escape it before the last line.

Guide project

A traffic light controller using FSM.


E x a m p l e

Traffic light

Port	Direction	Bus size	Description
clk	in	1	10MHz clock
rst_n	in	1	Active low asynchronous reset
en	in	1	Active high enable
red_light	out	1	Enable red light
yellow_light	out	1	Enable yellow light
green_light	out	1	Enable green light
display_led	out	16	7 segment display, 2 digits

Specification:

 - Clock frequency: 10MHz
- Control red (18s), yellow (3s), green light (15s)
- Control 7 segment light



ACTIVITY

Check 5.1, 5.2